

**Mechatronics Systems Design
Laboratory
ECE 491**

Igor Paprotny

Upcoming Checkout


- This week: - soldering lab (lab 1)
- Next week:
 - FRDM-KL25Z lab 2 (GPIO and ADC)
 - Altium Tutorial (Lab 3)
- BB up
- Project proposal due next Friday (project proposal guidelines on BB soon)

**DC Motors and Motor
Controllers**

- DC Motors
- FET review
- Motor controllers


DC Motors

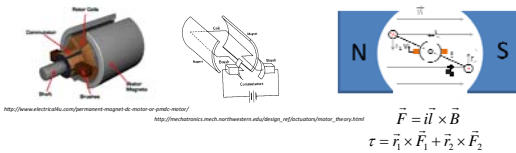- Use to provide a torque to a shaft, capable of spinning the shaft to some velocity under the application of a DC current



DC Motors

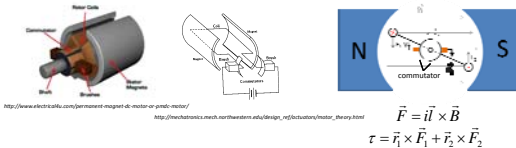
- Use to provide a torque to a shaft, capable of spinning the shaft to some velocity under the application of a DC current



Lorenz Law


Fleming's left-hand rule for motors

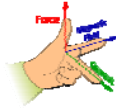- Left index finger is pointing in the direction of the magnetic field vector
- Left middle finger points in the direction of the current vector
- Thumb indicates the direction of the force




<http://www.bighoticons.com/forums/building/motor402>


DC Motors: commutator

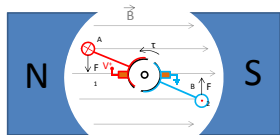


DC Motors: commutator

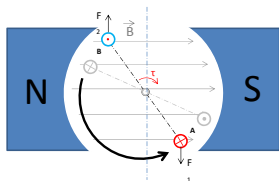

DC Motors: commutator

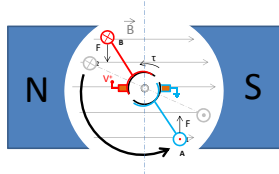


DC Motors: torque ripple

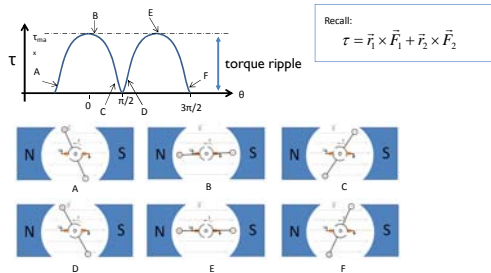


DC Motors: torque ripple

- 4-segment commutator:

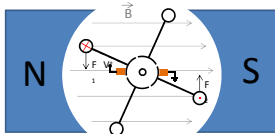


DC Motors: torque ripple

- 4-segment commutator:

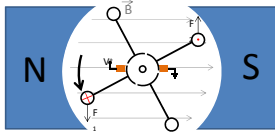


DC Motors: torque ripple

- 4-segment commutator:

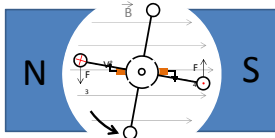


DC Motors: torque ripple

- 4-segment commutator:

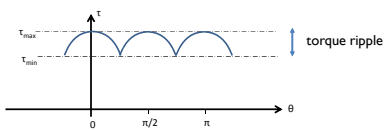


Now, greatly reduced torque ripple

Motor: Electrical Equivalent Circuit

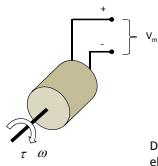


Symbol:

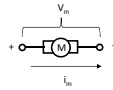

DC motor can be represented as an electrical element in a circuit diagram:


- V_m is the across element voltage (motor voltage)
- i_m is the through element current (motor current)

Motor: Electrical Equivalent Circuit

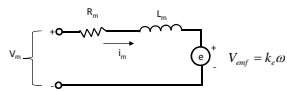


$$\tau = k_t i_m \quad V_m = k_f \omega + i_m R_m \quad \leftarrow \text{Assumes } \frac{di_m}{dt} \approx 0$$

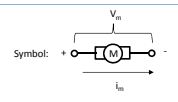An equivalent circuit can be constructed to model the operation of the motor from an electrical perspective.




Electromotive Force in a Wire moving through B-field

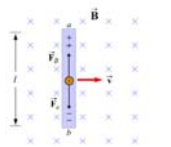Electrons in a wire moving through a magnetic field B at a velocity v will be pushed towards one end, while the holes will be pushed to the other end, causing a net potential V_{emf}




<http://web.mit.edu/8.021/www/materials/StudyGuide/guide10.pdf>


Motor: Electrical Equivalent Circuit

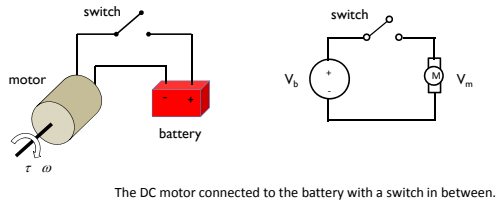


Motor: Electrical Equivalent Circuit

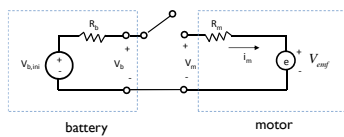

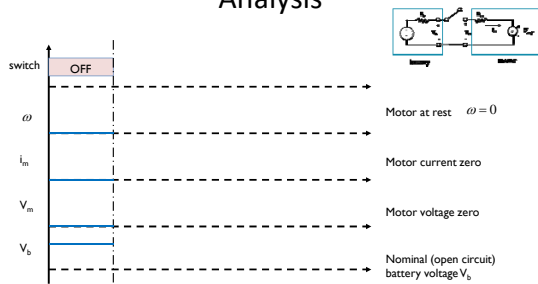
Motor: Electrical Equivalent Circuit Analysis



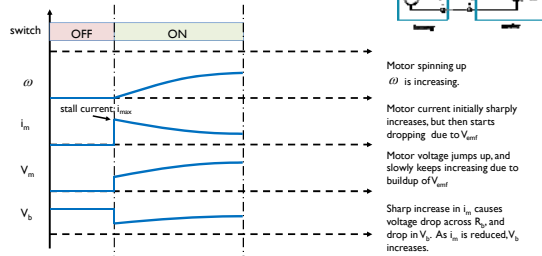
Motor: Electrical Equivalent Circuit Analysis



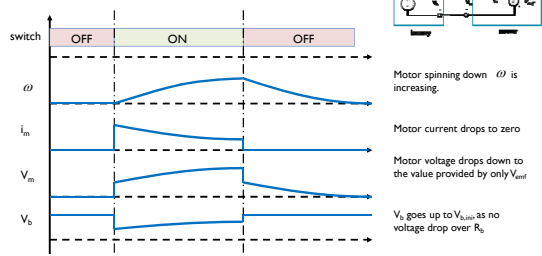Motor: Electrical Equivalent Circuit Analysis




Motor: Inductive Kickback

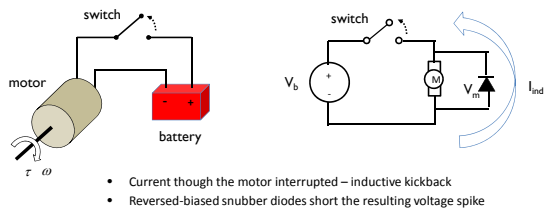

Summary: DC Motors

- DC Motors provide actuation for many mechatronic systems such as electric cars
- A commutator ensures that the torque spins the shaft in one direction for a certain polarity
- Back EMF generates a voltage across the winding, limiting the motor current, as a function of the angular velocity of the shaft (and winding)
- Two important implications of back EMF:
 - It will limit the ultimate angular velocity of the shaft (if it didn't all unloaded DC motors would likely disintegrate: $\omega \rightarrow \infty$)
 - Can be used for velocity sensing
 - Highest motor current at stall ($\omega = 0$). Motor controllers *must* be designed to handle stall currents
- Snubber diodes help to remove voltage spikes due to switching current through the winding


Motor Controllers

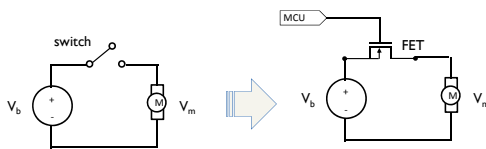


- Motor controller is an amplifier which converts the weak signals from microcontroller GPIO ports to high current that drive the motor.
- Solid-state using Power FET technology (e.g. NDP7060L)
 - Fast switching time
 - Large currents

Field Effect Transistor: A Review

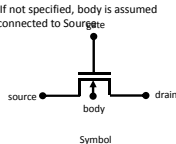- Can be n-channel or p-channel
 - Most common n-channel
- Fabricated on a doped silicon substrate
- Has four terminals: Source, Drain, Gate, and Body.
 - If not specified, body is assumed connected to Source



Symbol

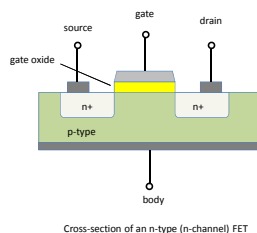


Cross-section of an n-type (n-channel) FET

Field Effect Transistor: A Review

FET Operation (n-channel)

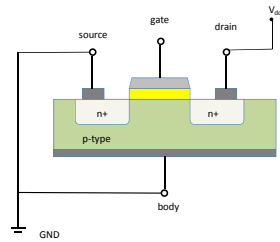
- source/body is usually connected to ground
- drain is connected to V_{dd}
- Initially source and drain isolated through a dual PN junction



Field Effect Transistor: A Review

FET Operation (n-channel)

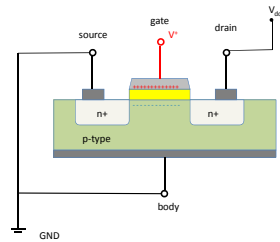
- To switch transistor on, gate is connected to positive voltage
- Accumulation of **positive** charges on the gate electrode attracts **negative** charges just underneath the gate, in the channel region



Field Effect Transistor: A Review

FET Operation (n-channel)

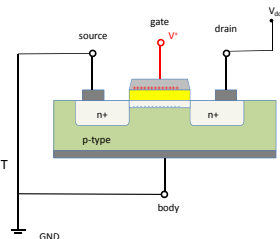
- When the density of negative charges in the channel reaches a certain threshold, the channel becomes conductive
 - Above gate threshold voltage
- Initially, channel acts like a resistor, FET operates in the **linear region**




Field Effect Transistor: A Review

FET Operation (n-channel)

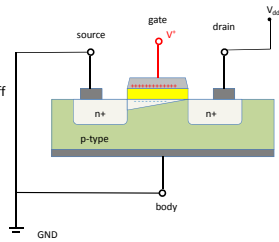
- As drain to source voltage (V_{ds}) increases, the channel gets pinched off at the drain, limiting the drain to source current (i_{ds})
- FET is now operating in the **saturation region**



Field Effect Transistor: A Review

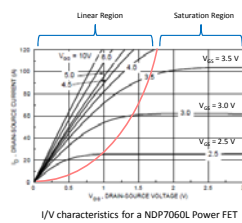

Datasheet NDP7060L

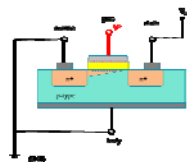

Summary: Field Effect Transistors

- Power FETs are used as solid state switches in a motor controller
- In an n-channel FET, positive charges on the gate form a n-type channel between the source and the drain
- Once on, a FET operates in either linear or saturated region
