


Mechatronics Systems Design Laboratory ECE 491

Igor Paprotny

Upcoming Checkout

- This week:
 - Altium Tutorial (Lab 3)
- Next week:
 - PWM (Lab 4)
 - Quiz 1 next Tuesday (2/14/2017)
- BB up
- Project proposal due Tuesday 2/14 (project proposal guidelines on BB soon)

Motor: Electrical Equivalent Circuit

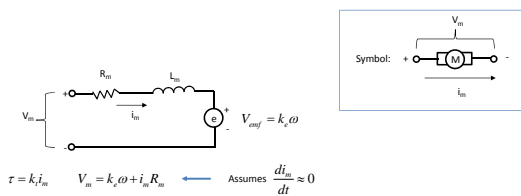


An equivalent circuit can be constructed to model the operation of the motor from an electrical perspective.

Field Effect Transistor: A Review


FET Operation (n-channel)

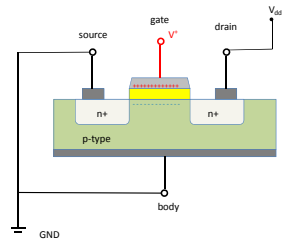- To switch transistor on, gate is connected to positive voltage
- Accumulation of **positive** charges on the gate electrode attracts **negative** charges just underneath the gate, in the channel region




Motor Controllers Topologies

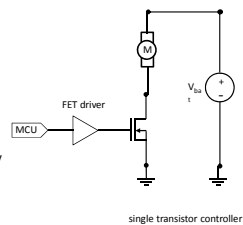- Single FET motor controllers have the simplest topology
 - Can only accelerate, and coast to stop
- Other topologies allow for:
 - Breaking
 - Backwards motion
- Most common, full H-bridge
- Possible to use a half-bridge to simplify the controller design




Motor Controllers Topology: Single FET

- FET ON
 - Accelerates

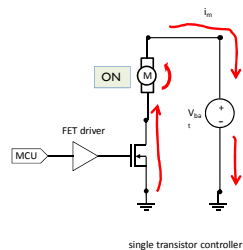


Motor Controllers Topology: Single FET

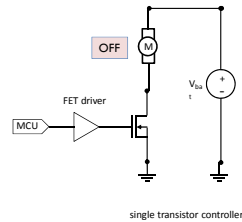- FET OFF
 - Coasts (open connectors) to stop




Motor Controllers Topology: Half-Bridge

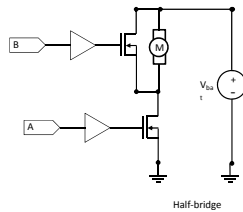- It is possible to accelerate breaking by use the concept of **dynamic breaking**
- The V_{emf} generated by the motor is used to drive current through armature to cause breaking of the motor
- Required additional FET




Motor Controllers Topology: Half-Bridge

- Accelerate:
 - A ON, B OFF

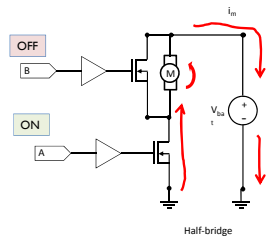


Motor Controllers Topology: Half-Bridge

- Dynamic Breaking:
 - A OFF, B ON

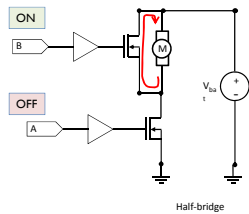


Motor Controllers Topology – H-Bridge

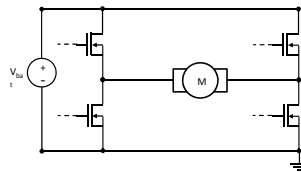- The most versatile motor controller topology is an H-bridge
- Requires four (4) FETs per motor




Motor Controllers Topology – H-Bridge

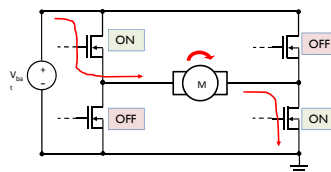- The most versatile motor controller topology
- Requires four (4) FETs per motor
- Supports:
 - Motion forward




Motor Controllers Topology – H-Bridge

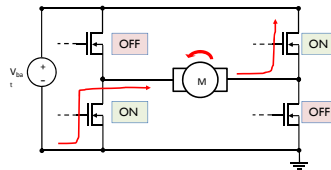- The most versatile motor controller topology
- Requires four (4) FETs per motor
- Supports:
 - Motion forward
 - Motion backward




Motor Controllers Topology – H-Bridge

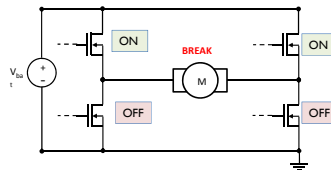- The most versatile motor controller topology
- Requires four (4) FETs per motor
- Supports:
 - Motion forward
 - Motion backward
 - Breaking




Motor Controllers Topology – H-Bridge

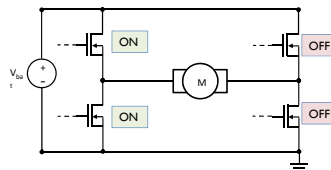- The most versatile motor controller topology
- Requires four (4) FETs per motor
- Supports:
 - Motion forward
 - Motion backward
 - Breaking
- Caution – H-bridge can short V_{dd} and ground



Motor Controllers Topology – H-Bridge

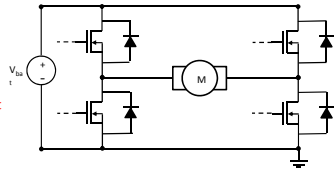- The most versatile motor controller topology
- Requires four (4) FETs per motor
- Supports:
 - Motion forward
 - Motion backward
 - Breaking
- **Caution – H-bridge can short V_{dd} and ground**
- Kick-back snubber diodes




Summary: Motor Controller Topology

- Single FET controller allows for acceleration (ON) or coasting (OFF)
- Half-bridge allows for acceleration, breaking, and coasting
- The most versatile motor controller configuration is an H-bridge
- H-bridge allows for
 - Motor actuation both back and forth
 - Dynamic breaking
- Careful not to short battery terminals in H-bridge !

Control for Autonomous Car Actuation

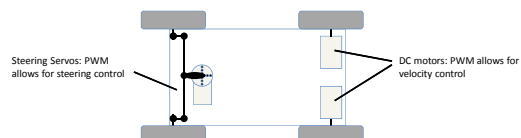- Autonomous car contains two main actuators
 - DC Motors: provide forward propulsion
 - Servos: provide steering
- Pulse-width modulation (PWM) allows for control of both




Pulse-Width Modulation (PWM): DC Motors

Pulse-Width Modulation (PWM) is used to vary torque produced by a motor while still using a driver FET only in either completely off or completely on states.

- Alternative (Bad approach):
 - Use the FET as a variable resistor
 - Large power dissipation by the FET

- Recall that: $\tau = k_t i_m$

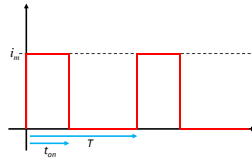- Pulse i_m by switching it fast on and off
 - Solid-state switch



Pulse-Width Modulation (PWM): DC Motors


Pulse-Width Modulation (PWM) is used to vary torque produced by a motor while still using a driver FET only in either completely off or completely on states.

- Alternative (Bad approach):
 - Use the FET as a variable resistor
 - Large power dissipation by the FET

- Recall that: $\tau = k_t i_m$

- Duty cycle: $d = \frac{t_{on}}{T}$
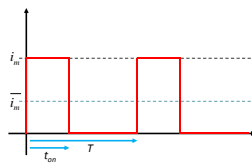
$$\bar{i}_m = d \cdot i_m \quad \Rightarrow \quad \bar{\tau} = k_t \cdot \bar{i}_m$$



RC Servo: Introduction

- RC servos
 - Initially developed for position control in radio-controlled RC applications
 - Low precision combination of DC motor and position feedback.
 - Currently used for other than RC applications in robotics, mechatronics





<https://www.hackmeister.dk/2010/07/controlling-an-rc-servo-with-an-fpga/>

RC Servo: Control

- Servo operation:
 - Most RC servo has three wires, almost universally color coded accordingly
 - » RED – supply voltage (V_{in}), 5 V.
 - » BLACK – Ground (GND)
 - » WHITE – Signal (S)
- Servo can typically rotate +/- 90 deg.
- Signal (S) causes the output shaft to rotate to a set position.
 - Position encoded in a pulse train provided to S
 - Period of 20 – 30 ms (typical)
 - Pulse 0.5 – 3 ms (typical)



RC Servo: PWM

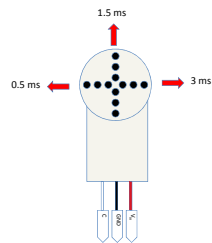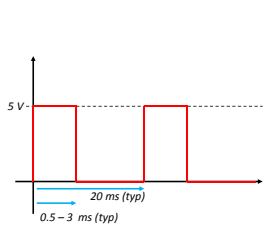

- Note: PWM in servo control different than for PWM in motors !

PWM using MCU

- Usually MCUs have ability to configure PWM for use with the GPIOs
 - Using timers to provide output PWM signal to both motors and servo
 - Independent channels per timer
 - Must be configured to assign timer and channel to a desired GPIO for output

Summary: PWM Motor and Servo Control

- Pulse-width modulation (PWM) is an efficient way of controlling power, and thus torque, of the motors
 - Can be used for velocity control
 - Avoids power drop over the FETs
 - **PWM duty-cycle** control the power
- Servos use an input pulse-train to control the direction of the output shaft
 - Can use PWM for control the direction of the servo
 - **PWM pulse duration** controls the direction
 - Must be calibrated

- Review of power supply for autonomous car
- Power Supply I: Linear Voltage Regulators
- Power Supply II: DC/DC converter
- Complete power supply solution


Review: Power Supply for Autonomous Car

- Different power needs for various sub-systems
- On-board power supply needed to:
 - Drive the motors (large currents)
 - Drive the servo (moderate currents)
 - Power the MCU (low currents, voltage stability)
 - Power the sensors (low currents, voltage stability)
- Battery is the main reservoir of on-board power
- Many battery types
 - Most common types for electric vehicles are Lithium ion batteries (high energy density, moderate cost, large discharge/charge cycle life)




<http://www.wirelessmadness.com/>

Review: Power Supply for Autonomous Car

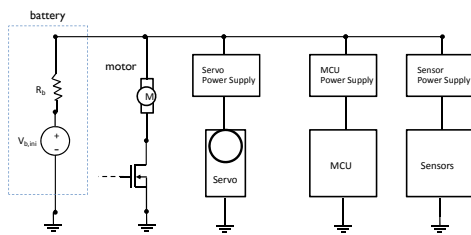

Schematic of the required power supply for the sub-systems


Review: Power Supply for Autonomous Car

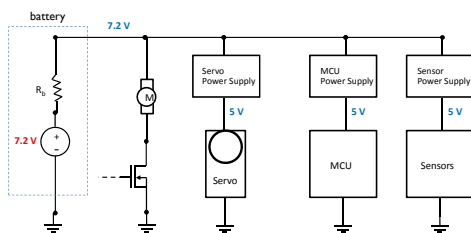


Schematic of the required power supply for the sub-systems

Power Supply 1: Linear Voltage Regulator

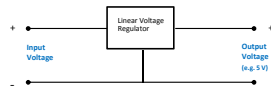
- Reduces the supply voltage to a stable value set value
 - Output voltage less than input voltage
 - A variable (controlled) resistor
- Key parameters
 - Output voltage (e.g. 5 V)
 - Input voltage range
 - Output current
 - Dropout
- E.g.: LM2940CT-5.0/NOPB
 - 5 Vout
 - 0V to 26V input
 - 1 A max output
 - 500mV Dropout




Power Supply 1: Linear Voltage Regulator

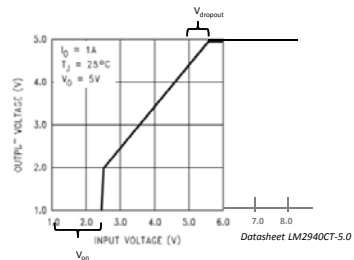

Review: Power Supply for Autonomous Car

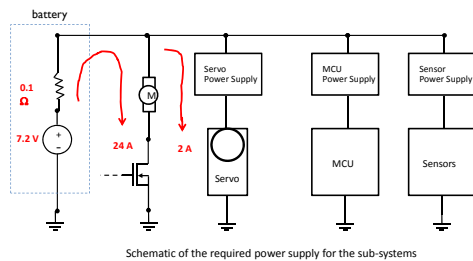

Review: Power Supply for Autonomous Car

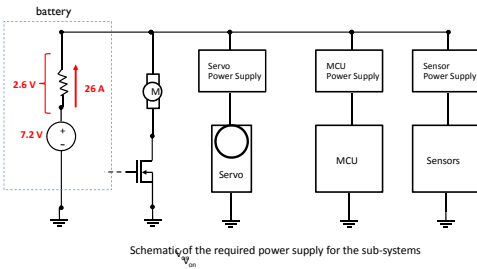


Power Supply II: DC/DC Converter


- Must elevate the voltage to provide a stable power supply (say 5 V)
- This can be done using switching power supplies
- Switching power supply:
 - Uses capacitors or inductors to store energy
 - Switches between a charge and discharge cycle
 - During the discharge cycle the energy is added or subtracted from the input voltage
 - Boost converter adds the stored voltage to boost supply voltage
 - Buck converters subtract the stored voltage to decrease the supply voltage
- This class will design a boost converter

Power Supply II: Boost Converter

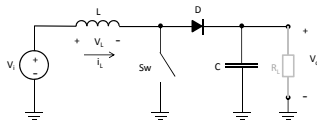
- Used to boost the input voltage
- Uses a storage inductor as the storage element for the boost stage



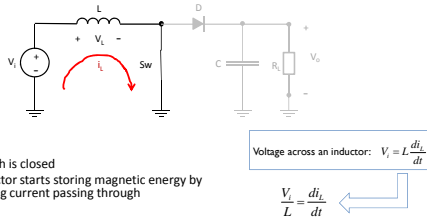
Power Supply II: Boost Converter – 1 Charge Stage



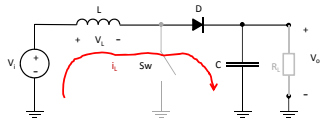
Power Supply II: Boost Converter – 2 Step-up Stage



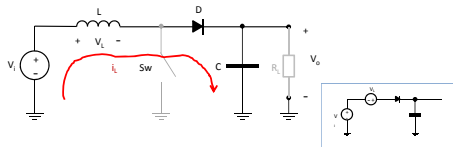Power Supply II: Boost Converter – 2 Step-up Stage




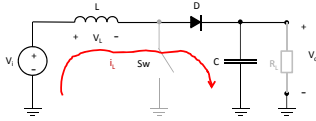Power Supply II: Boost Converter – 2 Step-up Stage




- The step-up current (slope) through the inductor is now: $\frac{V_i - V_o}{L} = \frac{di_L}{dt}$
- Inductor is discharging

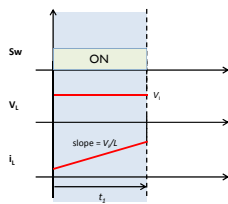Power Supply II: Boost Converter – Charge Step Revisited



The inductor is charging up.
After t_1 we open the switch
(Sw → OFF).

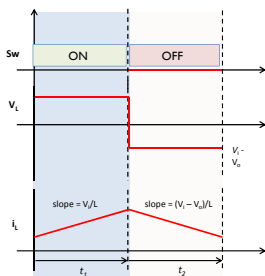Power Supply II: Boost Converter – Step-Up Step Revisited




The inductor is charging up.
After t_1 we open the switch
(Sw → OFF).

The inductor is now dis-
charging and transf. Aftg
charge to capacitor C for the
duration of t_2 .


Power Supply for Autonomous Car – Entire System

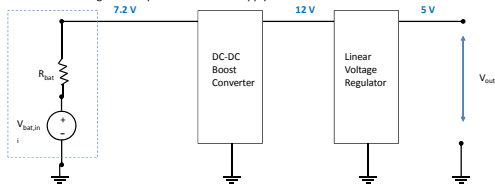- Two-component stable power-supply:
 - Boost converter to make sure input voltage to linear regulator is always $> 5\text{ V} + V_{\text{dropout}}$
 - E.g. 12 V
 - Linear regulator to provide stable 5 V supply




Power Supply for Autonomous Car – Entire System

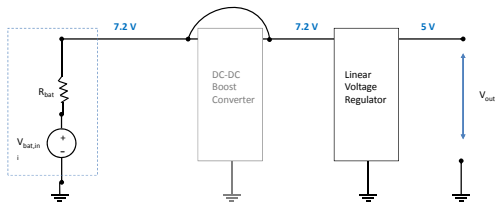
- Redundancy:
 - Reliability through redundancy – can disconnect the DC-DC converter and still most likely be ok.
 - Can avoid high current conditions in SW





Power Supply for Autonomous Car – Entire System

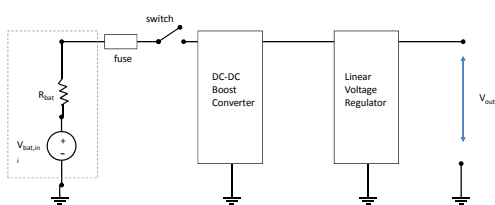- Finishing it up:
 - Fuse (battery protection)
 - Emergency stop switch



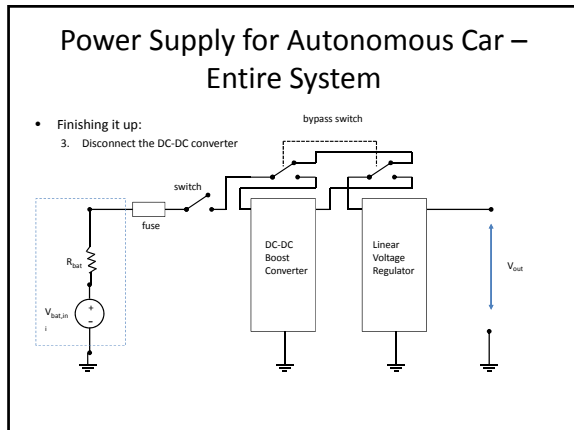

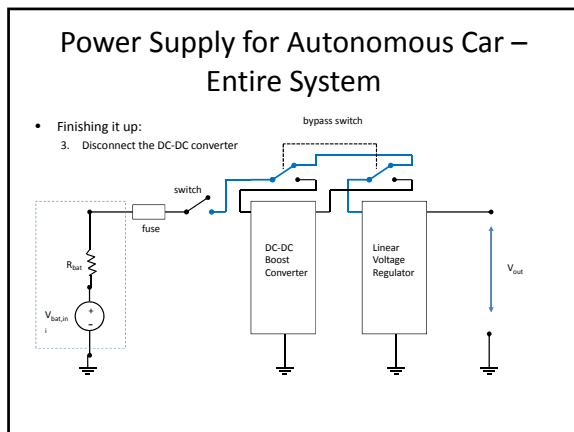

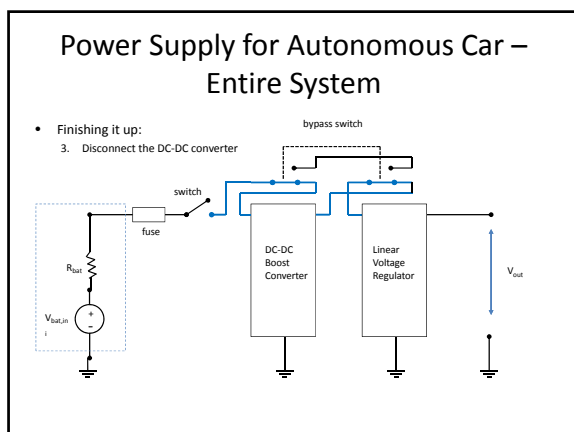

Summary: Power Supply for Autonomous Car

- Reliable supply necessary to provide different voltage or current to car sub-systems
- Output battery voltage can vary as a function of current
 - Can cause problems at stall, turning
- Linear Voltage Regulator can provide a stable output voltage
 - As long and $V_{out} > V_{in} + V_{dropout}$
- A switching (DC-DC) converter can both reduce or increase the voltage a desired level
- A DC-DC boost converter, together with one or more linear voltage regulator, can provide a stable supply voltage
