

**Mechatronics Systems Design
Laboratory
ECE 491**

Igor Paprotny

Upcoming Checkout


- This week:
 - FRDM-KL25Z lab 2 (GPIO and ADC)
- Next week:
 - PWM (Lab 3)
 - Altium Tutorial (Lab 4)
- BB up
- Project proposal due next Friday (project proposal guidelines on BB soon)

**DC Motors and Motor
Controllers**

- DC Motors
- FET review
- Motor controllers

DC Motors

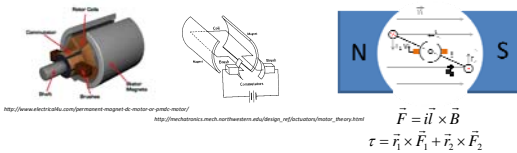
- Use to provide a torque to a shaft, capable of spinning the shaft to some velocity under the application of a DC current




$$\vec{F} = i\vec{l} \times \vec{B}$$

$$\tau = \vec{r}_1 \times \vec{F}_1 + \vec{r}_2 \times \vec{F}_2$$


DC Motors: commutator

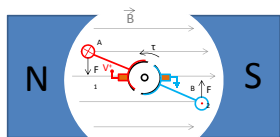


DC Motors: commutator

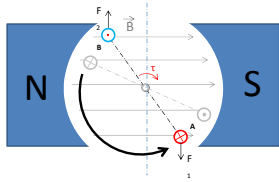

Motor: Electrical Equivalent Circuit

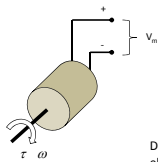



Symbol:

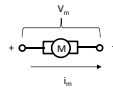

DC motor can be represented as an electrical element in a circuit diagram:

- V_m is the across element voltage (motor voltage)
- i_m is the through element current (motor current)

Motor: Electrical Equivalent Circuit

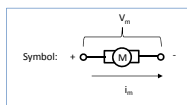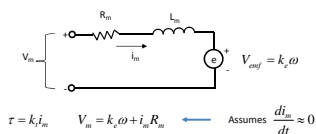


An equivalent circuit can be constructed to model the operation of the motor from an electrical perspective.

Summary: DC Motors

- DC Motors provide actuation for many mechatronic systems such as electric cars
- A commutator ensures that the torque spins the shaft in one direction for a certain polarity
- Back EMF generates a voltage across the winding, limiting the motor current, as a function of the angular velocity of the shaft (and winding)
- Two important implications of back EMF:
 - It will limit the ultimate angular velocity of the shaft (if it didn't all unloaded DC motors would likely disintegrate: $\omega \rightarrow \infty$)
 - Can be used for velocity sensing
 - Highest motor current at stall ($\omega = 0$). Motor controllers *must* be designed to handle stall currents
- Snubber diodes help to remove voltage spikes due to switching current through the winding


Motor Controllers

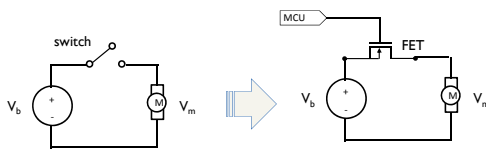


- Motor controller is an amplifier which converts the weak signals from microcontroller GPIO ports to high current that drive the motor.
- Solid-state using Power FET technology (e.g. NDP7060L)
 - Fast switching time
 - Large currents

Field Effect Transistor: A Review

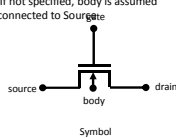- Can be n-channel or p-channel
 - Most common n-channel
- Fabricated on a doped silicon substrate
- Has four terminals: Source, Drain, Gate, and Body.
 - If not specified, body is assumed connected to Source



Symbol

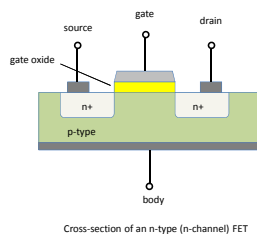


Cross-section of an n-type (n-channel) FET

Field Effect Transistor: A Review

FET Operation (n-channel)

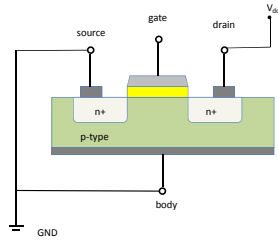
- source/body is usually connected to ground
- drain is connected to V_{dd}
- Initially source and drain isolated through a dual PN junction



Field Effect Transistor: A Review

FET Operation (n-channel)

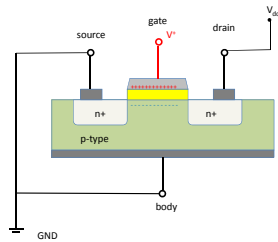
- To switch transistor on, gate is connected to positive voltage
- Accumulation of **positive** charges on the gate electrode attracts **negative** charges just underneath the gate, in the channel region



Field Effect Transistor: A Review

FET Operation (n-channel)

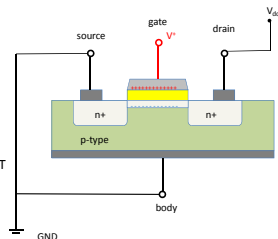
- When the density of negative charges in the channel reaches a certain threshold, the channel becomes conductive
 - Above gate threshold voltage
- Initially, channel acts like a resistor, FET operates in the **linear region**




Field Effect Transistor: A Review

FET Operation (n-channel)

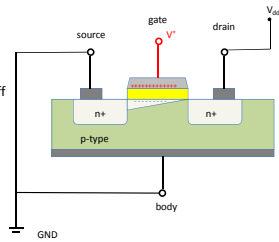- As drain to source voltage (V_{ds}) increases, the channel gets pinched off at the drain, limiting the drain to source current (i_{ds})
- FET is now operating in the **saturation region**




Field Effect Transistor: A Review

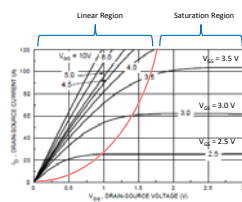

I/V characteristics for a NDP7060L Power FET

Datasheet NDP7060L

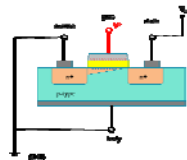


Summary: Field Effect Transistors

- Power FETs are used as solid state switches in a motor controller
- In an n-channel FET, positive charges on the gate form a n-type channel between the source and the drain
- Once on, a FET operates in either linear or saturated region


Motor Controllers: FETS as switches

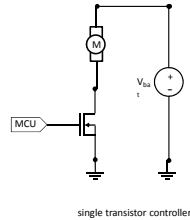- Switch is now replaced with a FET
- Single FET motor controller
 - Only turn in one direction
- Motor and battery resistance in series
 - Analyze for maximum (i.e. stall) current





Motor Controllers: FETS as switches

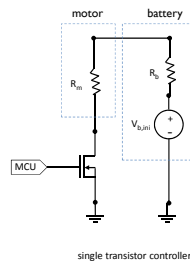- Modify electric diagram for stall ($\omega = 0$)
 - No back EMF
 - No inductive component
- Load-line analysis




Motor Controllers: FETS as switches

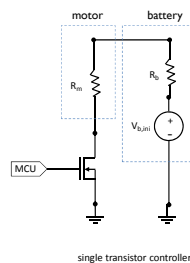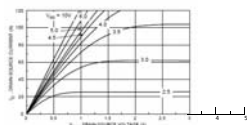- E.g. assume
 - $V_{bat} = 5\text{ V}$, $R_m = 0.4\ \Omega$, $R_b = 0.1\ \Omega$
 - V_{gs} provided by the MCU




Motor Controllers: FETS as switches

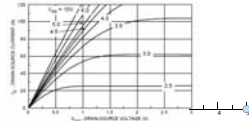- E.g. assume
 - $V_{ds,sat} = 5\text{ V}$, $R_{on} = 0.4\ \Omega$, $R_b = 0.1\ \Omega$
 - V_{gs} provided by the MCU



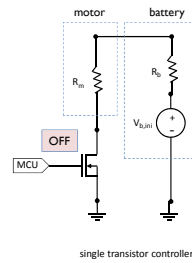
I/V characteristics for a NDP7060L Power FET
Datasheet NDP7060L




single transistor controller

Motor Controllers: FETS as switches

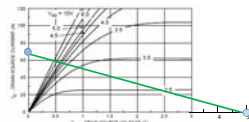- E.g. assume
 - $V_{ds,sat} = 5\text{ V}$, $R_{on} = 0.06\ \Omega$, $R_b = 0.01\ \Omega$
 - V_{gs} provided by the MCU



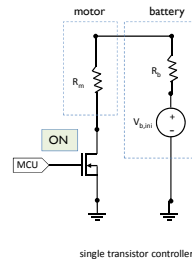
I/V characteristics for a NDP7060L Power FET
Datasheet NDP7060L




single transistor controller

Motor Controllers: FETS as switches

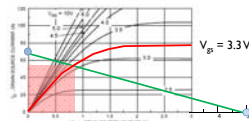- E.g. assume
 - $V_{ds,sat} = 5\text{ V}$, $R_{on} = 0.06\ \Omega$, $R_b = 0.01\ \Omega$
 - V_{gs} provided by the MCU




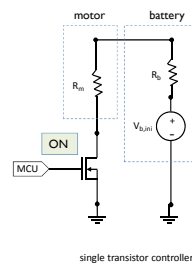
I/V characteristics for a NDP7060L Power FET
Datasheet NDP7060L



single transistor controller

Motor Controllers: FETS as switches

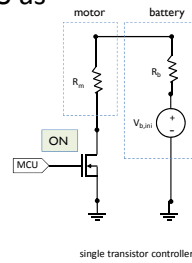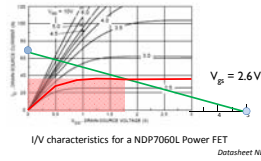
- E.g. assume
 - $V_{ds(on)} = 5\text{ V}$, $R_{ds(on)} = 0.06\ \Omega$, $R_b = 0.01\ \Omega$
 - V_{gs} provided by the MCU



single transistor controller



Motor Controllers: the need for FET drivers

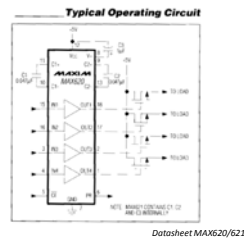- To reduce the power dissipation in ON state, V_{gs} must be as high as possible (up to gate voltage breakdown)
 - V_{gs} may be above V_{ds}
- 3.3 V output from GPIO not high enough
- Solution: FET Drivers
 - Solid-state circuits that elevate ON output voltage to a higher ON level.
 - In some cases much higher than V_{ds}
 - E.g. MAX 621 elevates ON output voltage by 11 V above V_{ds} .



Motor Controllers: FETS as switches

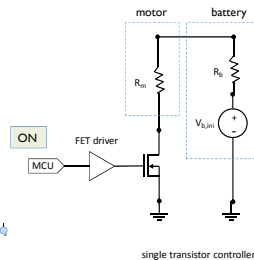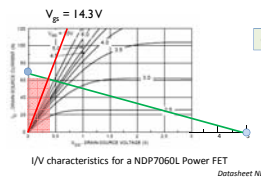- E.g. assume
 - $V_{ds(on)} = 5\text{ V}$, $R_{ds(on)} = 0.06\ \Omega$, $R_b = 0.01\ \Omega$
 - V_{gs} provided by the MCU



single transistor controller

Summary: Motor Controllers

- Motor controllers are used to control the actuation of a motor using one or more FETs
- Load-line analysis is used to determine power dissipated in a FET in a motor controller
- To lower dissipated power in FET, V_{GS} needs to be as high as possible
- A FET driver is used to elevate V_{GS} above $V_{GS,th}$ ensuring proper switching


Mechatronics Systems Design Laboratory ECE 491

Motor Control, PWM and Servo
Control

- Motor controller topologies
- PWM for motor (velocity) control
- Review of servo operation
- PWM for servo (steering) control


Motor Controllers Topologies

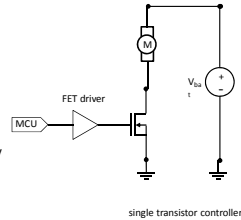- Single FET motor controllers have the simplest topology
 - Can only accelerate, and coast to stop
- Other topologies allow for:
 - Breaking
 - Backwards motion
- Most common, full H-bridge
- Possible to use a half-bridge to simplify the controller design




Motor Controllers Topology: Single FET

- FET ON
 - Accelerates

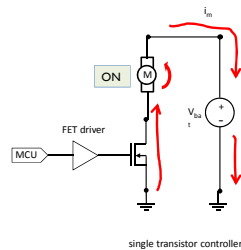


Motor Controllers Topology: Single FET

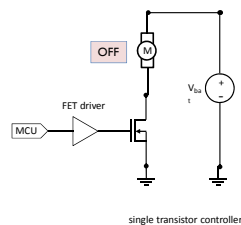- FET OFF
 - Coasts (open connectors) to stop




Motor Controllers Topology: Half-Bridge

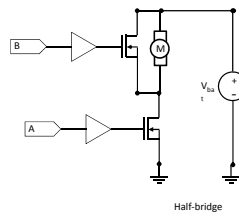- It is possible to accelerate breaking by use the concept of **dynamic breaking**
- The V_{bus} generated by the motor is used to drive current through armature to cause breaking of the motor
- Required additional FET




Motor Controllers Topology: Half-Bridge

- Accelerate:
— A ON, B OFF

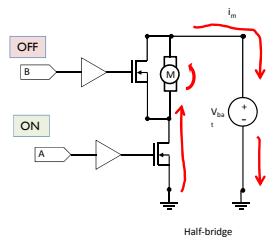


Motor Controllers Topology: Half-Bridge

- Dynamic Breaking:
— A OFF, B ON

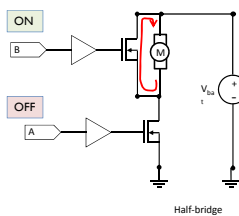


Motor Controllers Topology – H-Bridge

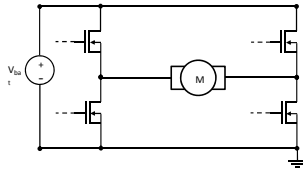- The most versatile motor controller topology is an H-bridge
- Requires four (4) FETs per motor




Motor Controllers Topology – H-Bridge

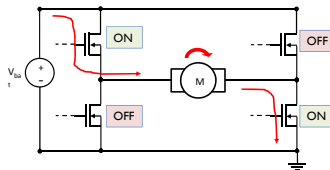- The most versatile motor controller topology
- Requires four (4) FETs per motor
- Supports:
 - Motion forward




Motor Controllers Topology – H-Bridge

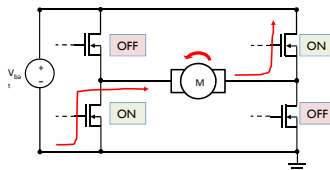- The most versatile motor controller topology
- Requires four (4) FETs per motor
- Supports:
 - Motion forward
 - Motion backward




Motor Controllers Topology – H-Bridge

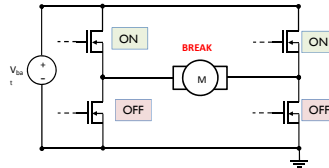- The most versatile motor controller topology
- Requires four (4) FETs per motor
- Supports:
 - Motion forward
 - Motion backward
 - Breaking




Motor Controllers Topology – H-Bridge

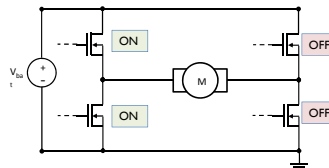- The most versatile motor controller topology
- Requires four (4) FETs per motor
- Supports:
 - Motion forward
 - Motion backward
 - Breaking
- Caution – H-bridge can short V_{in} and ground



Motor Controllers Topology – H-Bridge

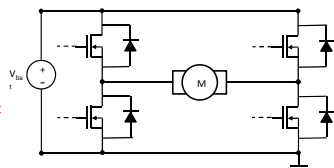- The most versatile motor controller topology
- Requires four (4) FETs per motor
- Supports:
 - Motion forward
 - Motion backward
 - Breaking
- Caution – H-bridge can short V_{in} and ground
- Kick-back snubber diodes




Summary: Motor Controller Topology

- Single FET controller allows for acceleration (ON) or coasting (OFF)
- Half-bridge allows for acceleration, braking, and coasting
- The most versatile motor controller configuration is an H-bridge
- H-bridge allows for
 - Motor actuation both back and forth
 - Dynamic braking
- Careful not to short battery terminals in H-bridge !

Control for Autonomous Car Actuation

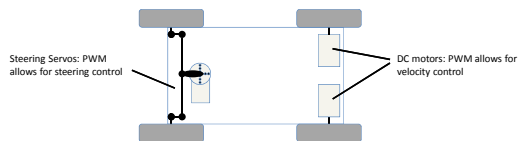- Autonomous car contains two main actuators
 - DC Motors: provide forward propulsion
 - Servos: provide steering
- Pulse-width modulation (PWM) allows for control of both




Pulse-Width Modulation (PWM): DC Motors

Pulse-Width Modulation (PWM) is used to vary torque produced by a motor while still using a driver FET only in either completely off or completely on states.

- Alternative (Bad approach):
 - Use the FET as a variable resistor
 - Large power dissipation by the FET

Recall that: $\tau = k_f i_m$

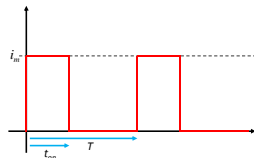- Pulse i_m by switching it fast on and off
 - Solid-state switch



Pulse-Width Modulation (PWM): DC Motors


Pulse-Width Modulation (PWM) is used to vary torque produced by a motor while still using a driver FET only in either completely off or completely on states.

- Alternative (Bad approach):
 - Use the FET as a variable resistor
 - Large power dissipation by the FET

Recall that: $\tau = k_t i_m$

Duty cycle: $d = \frac{t_{on}}{T}$
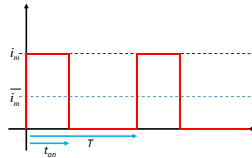
$$\bar{i}_m = d \cdot i_m \implies \bar{\tau} = k_t \cdot \bar{i}_m$$



RC Servo: Introduction

- RC servos
 - Initially developed for position control in radio-controlled RC applications
 - Low precision combination of DC motor and position feedback.
 - Currently used for other than RC applications in robotics, mechatronics




<https://www.hackmeister.dk/2010/07/controlling-an-rc-servo-with-an-fpga/>

RC Servo: Control

- Servo operation:
 - Most RC servo has three wires, almost universally color coded accordingly
 - RED – supply voltage (Vin), 5 V.
 - BLACK – Ground (GND)
 - WHITE – Signal (S)
- Servo can typically rotate +/- 90 deg.
- Signal (S) causes the output shaft to rotate to a set position.
 - Position encoded in a pulse train provided to S
 - Period of 20 – 30 ms (typical)
 - Pulse 0.5 – 3 ms (typical)



RC Servo: PWM

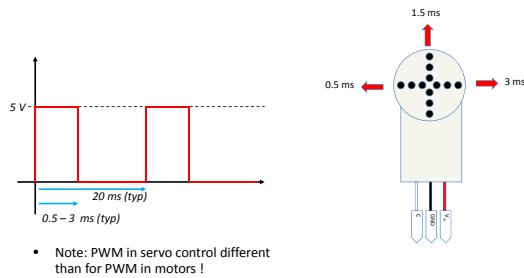

PWM using MCU

- Usually MCUs have ability to configure PWM for use with the GPIOs
 - Using timers to provide output PWM signal to both motors and servo
 - Independent channels per timer
 - Must be configured to assign timer and channel to a desired GPIO for output

Summary: PWM Motor and Servo Control

- Pulse-width modulation (PWM) is an efficient way of controlling power, and thus torque, of the motors
 - Can be used for velocity control
 - Avoids power drop over the FETs
 - PWM duty-cycle** control the power
- Servos use an input pulse-train to control the direction of the output shaft
 - Can use PWM for control the direction of the servo
 - PWM pulse duration** controls the direction
 - Must be calibrated