


Mechatronics Systems Design Laboratory ECE 491

Igor Paprotny

Upcoming Checkout

- This week:
 - Altium Tutorial (Lab 4)
- Next week:
 - Motor controller – Using MAX620

Motor: Electrical Equivalent Circuit

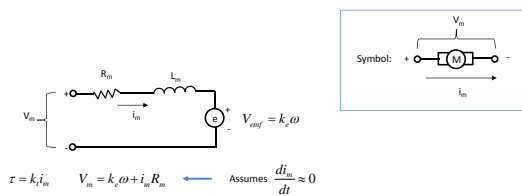


An equivalent circuit can be constructed to model the operation of the motor from an electrical perspective.

Field Effect Transistor: A Review


FET Operation (n-channel)

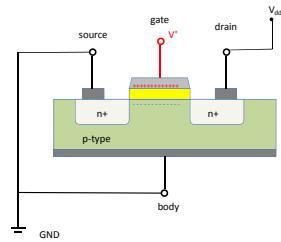- To switch transistor on, gate is connected to positive voltage
- Accumulation of **positive** charges on the gate electrode attracts **negative** charges just underneath the gate, in the channel region




Motor Controllers Topologies

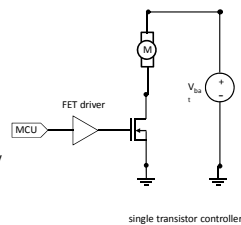- Single FET motor controllers have the simplest topology
 - Can only accelerate, and coast to stop
- Other topologies allow for:
 - Breaking
 - Backwards motion
- Most common, full H-bridge
- Possible to use a half-bridge to simplify the controller design




Motor Controllers Topology: Half-Bridge

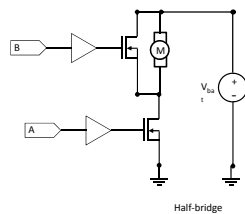- It is possible to accelerate breaking by use the concept of **dynamic breaking**
- The V_{emf} generated by the motor is used to drive current through armature to cause breaking of the motor
- Required additional FET



Motor Controllers Topology – H-Bridge

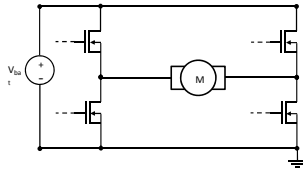- The most versatile motor controller topology is an H-bridge
- Requires four (4) FETs per motor




- Review of power supply for autonomous car
- Power Supply I: Linear Voltage Regulators
- Power Supply II: DC/DC converter
- Complete power supply solution

Review: Power Supply for Autonomous Car


- Different power needs for various sub-systems
- On-board power supply needed to:
 - Drive the motors (large currents)
 - Drive the servo (moderate currents)
 - Power the MCU (low currents, voltage stability)
 - Power the sensors (low currents, voltage stability)
- Battery is the main reservoir of on-board power
- Many battery types
 - Most common types for electric vehicles are Lithium ion batteries (high energy density, moderate cost, large discharge/charge cycle life)



Review: Power Supply for Autonomous Car

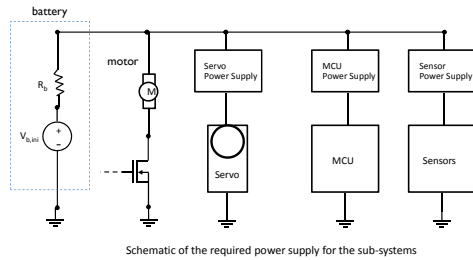


Review: Power Supply for Autonomous Car

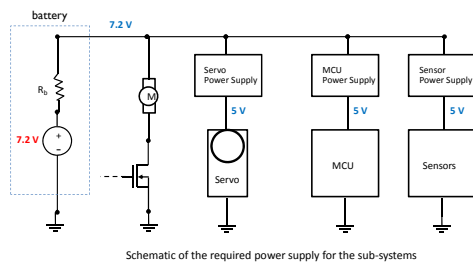


Power Supply 1: Linear Voltage Regulator

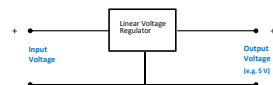
- Reduces the supply voltage to a stable value set value
 - Output voltage less than input voltage
 - A variable (controlled) resistor
- Key parameters
 - Output voltage (e.g. 5 V)
 - Input voltage range
 - Output current
 - Dropout
- E.g.: LM2940CT-5.0/NOPB
 - 5 Vout
 - 0V to 26V input
 - 1 A max output
 - 500mV Dropout




Power Supply 1: Linear Voltage Regulator

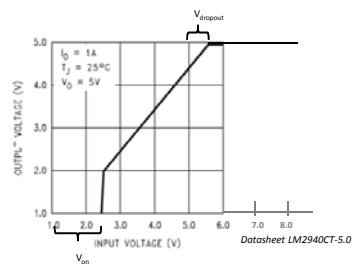

Review: Power Supply for Autonomous Car

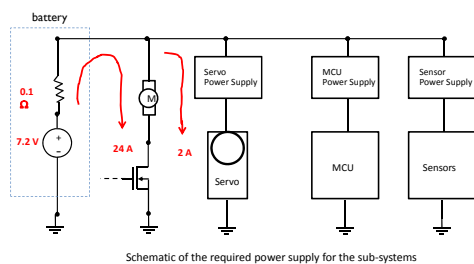

Review: Power Supply for Autonomous Car

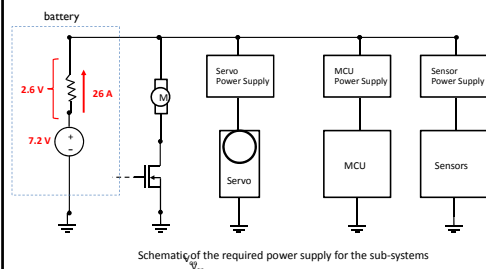


Power Supply II: DC/DC Converter


- Must elevate the voltage to provide a stable power supply (say 5 V)
- This can be done using switching power supplies
- Switching power supply:
 - Uses capacitors or inductors to store energy
 - Switches between a charge and discharge cycle
 - During the discharge cycle the energy is added or subtracted from the input voltage
 - Boost converter adds the stored voltage to boost supply voltage
 - Buck converters subtract the stored voltage to decrease the supply voltage
- This class will design a boost converter

Power Supply II: Boost Converter

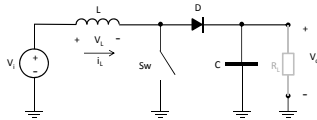- Used to boost the input voltage
- Uses a storage inductor as the storage element for the boost stage



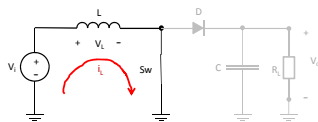Power Supply II: Boost Converter – 1 Charge Stage




- The switch is closed
- The inductor starts storing magnetic energy by conserving current passing through

Voltage across an inductor: $V_L = L \frac{di_L}{dt}$


$$\frac{V_L}{L} = \frac{di_L}{dt}$$

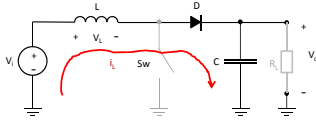Power Supply II: Boost Converter – 2 Step-up Stage




- The switch opens
- Inductor "attempts" to maintain current and thus throws large inverted voltage to maintain current i_L .
- The current i_L passes through diode D and charges up capacitor C

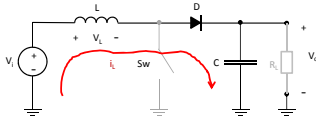Power Supply II: Boost Converter – 2 Step-up Stage




- The switch opens
- Inductor "attempts" to maintain current and thus throws large inverted voltage to maintain current i_L .
- The current i_L passes through diode D and charges up capacitor C

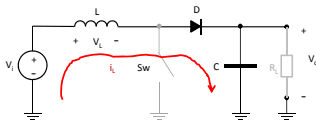Power Supply II: Boost Converter – 2 Step-up Stage




- The step-up current (slope) through the inductor is now: $\frac{V_i - V_o}{L} = \frac{di_L}{dt}$
- Inductor is discharging

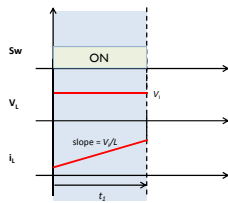Power Supply II: Boost Converter – Charge Step Revisited



The inductor is charging up.
After t_1 we open the switch
(Sw \rightarrow OFF).

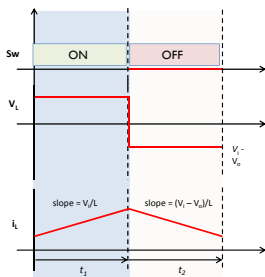
Power Supply II: Boost Converter – Step-Up Step Revisited



The inductor is charging up.
After t_1 we open the switch
(Sw \rightarrow OFF).

The inductor is now discharging and transf. Aftng
charge to capacitor C for the
duration of t_2 .

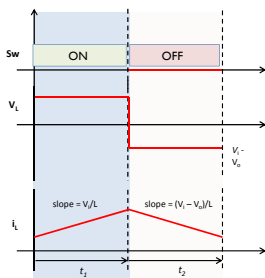Power Supply II: Boost Converter – Step-Up Step Revisited




The inductor is charging up.
After t_1 we open the switch
(Sw \rightarrow OFF).

The inductor is now discharging and transf. Aftng
charge to capacitor C for the
duration of t_2 .

At steady state:
$$V_o = \frac{V_i}{\left(\frac{t_2}{t_2 + t_1} \right)}$$


Power Supply for Autonomous Car – Entire System

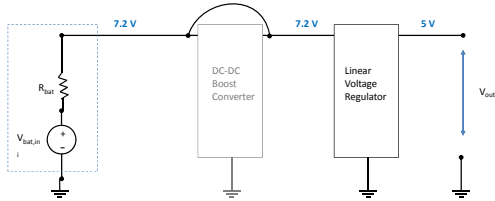- Redundancy:
 - Reliability through redundancy – can disconnect the DC-DC converter and still most likely be ok.
 - Can avoid high current conditions in SW




Power Supply for Autonomous Car – Entire System

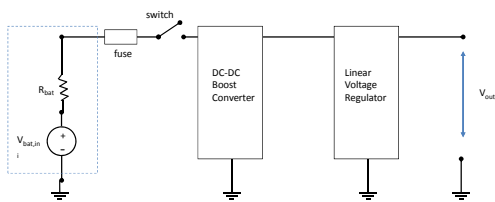- Finishing it up:
 - Fuse (battery protection)
 - Emergency stop switch



Power Supply for Autonomous Car – Entire System

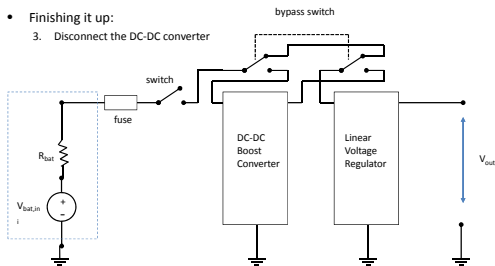
- Finishing it up:
 - Disconnect the DC-DC converter



Power Supply for Autonomous Car – Entire System

- Finishing it up:


3. Disconnect the DC-DC converter

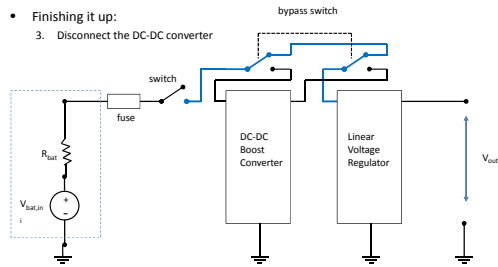

Power Supply for Autonomous Car – Entire System

- Finishing it up:

3. Disconnect the DC-DC converter

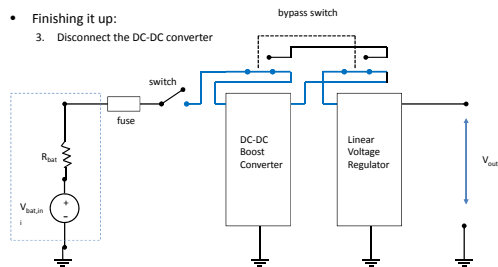


Summary: Power Supply for Autonomous Car

- Reliable supply necessary to provide different voltage or current to car sub-systems
- Output battery voltage can vary as a function of current
 - Can cause problems at stall, turning
- Linear Voltage Regulator can provide a stable output voltage
 - As long and $V_{out} > V_{in} + V_{dropout}$
- A switching (DC-DC) converter can both reduce or increase the voltage a desired level
- A DC-DC boost converter, together with one or more linear voltage regulator, can provide a stable supply voltage

Sensing


Sensors - An Introduction

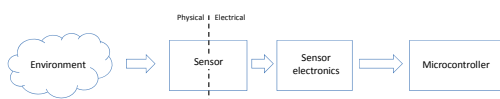- Obtains the information about the environment
- Provides transduction between the physical (mechanical) and electrical domains
 - Transduction: Conversion of energy between energy domains



Sensors - An Introduction

- Relevant types of sensors:

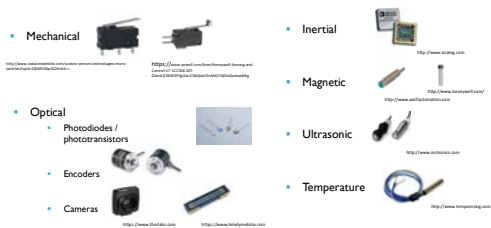


Review – Operational Amplifiers

- Operational Amplifiers (OpAmps) are commonly used to amplify (precondition) sensing signal for input to a microcontrollers
- OpAmps are analyzed as *ideal*



Ideal OP-Amp: $V_{out} = A(V^+ - V^-)$

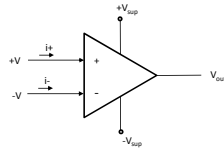- High input impedance ($i^+ \approx 0$, $i^- \approx 0$)
- Low output impedance
- Infinite gain (A is very large)




Review – Operational Amplifiers

- Two main configurations:

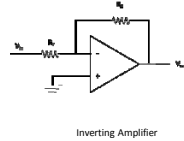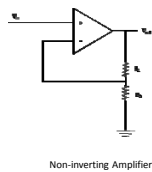


Review – Operational Amplifiers

- Non-Inverting OpAmp

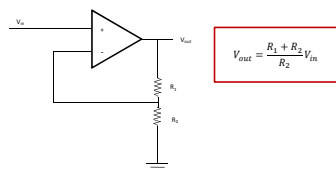

Review – Operational Amplifiers


- Inverting OpAmp

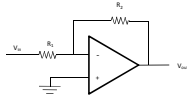

$$V_{out} = -\frac{R_2}{R_1} V_{in}$$

Review – Operational Amplifiers



- Inverting OpAmp as charge integrator

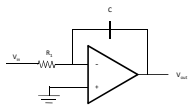

$$V_{out}(t') = -\int_0^{t'} \frac{V_{in}(t)}{RC} dt + V_{out}(0)$$

Review – Operational Amplifiers

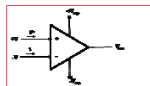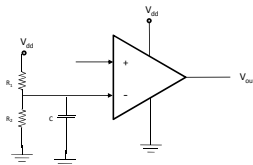- Single supply inverting OpAmp
 - Need to create a virtual ground at $\frac{1}{2} V_{dd}$



Summary: Sensors and Operational Amplifiers

- Sensors provide information about the state of the Environment to the microcontroller
- Operational Amplifiers (OpAmps) are often used to amplify the sensing signal
- OpAmps come in two flavors
 - Non-inverting
 - Inverting
- Gain of a non-inverting amplifier is always > 1
- A virtual ground can be used if an amplifier is used as single supply
