

Mechatronics Systems Design
Laboratory
ECE 491

Igor Paprotny

Upcoming Checkout

- This week:
 - Motor controller – Using MAX620 (Lab 5)
- Next week:
 - DC – DC Converter – Lab 6

Quiz 2 (2/28/2017)

- 30 min at start of class
- Topics:
 - DC-DC converter
 - OP-Amps
 - Encoders (incl. today)

PCB Board 1


- Designs to John by Wednesday 3/8/2017
 - Noon
- Use template provided for you
- Shall contain:
 - power supply (DC-DC)
 - Remember disconnect switch
 - Motor controllers

Midterm (3/14/2017)

- Open Book/Open Notes
- Topics:
 - Motors
 - Motor controllers
 - FET review
 - DC-DC converter
 - OP-Amps review
 - Encoders (incl. today)


Motor Controllers Topologies

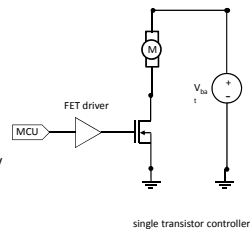- Single FET motor controllers have the simplest topology
 - Can only accelerate, and coast to stop
- Other topologies allow for:
 - Breaking
 - Backwards motion
- Most common, full H-bridge
- Possible to use a half-bridge to simplify the controller design




Motor Controllers Topology: Half-Bridge

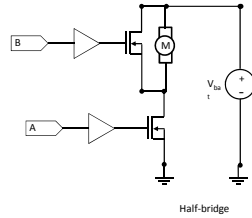- It is possible to accelerate breaking by use the concept of **dynamic breaking**
- The V_{emf} generated by the motor is used to drive current through armature to cause breaking of the motor
- Required additional FET




Motor Controllers Topology – H-Bridge

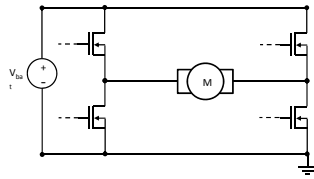
- The most versatile motor controller topology is an H-bridge
- Requires four (4) FETs per motor



Review: Power Supply for Autonomous Car

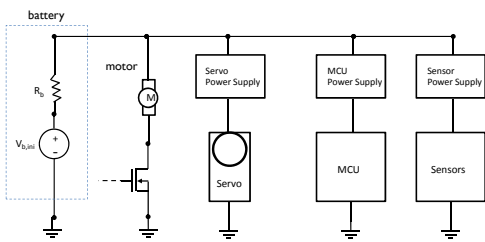

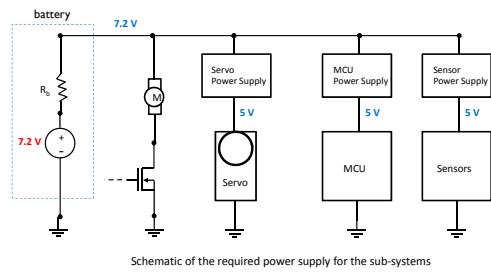
Schematic of the required power supply for the sub-systems



- Reduces the supply voltage to a stable value set value
 - Output voltage less than input voltage
 - A variable (controlled) resistor
- Key parameters
 - Output voltage (e.g. 5 V)
 - Input voltage range
 - Output current
 - Dropout
- E.g.: LM2940CT-5.0/NOPB
 - 5 Vout
 - 0V to 26V input
 - 1 A max output
 - 500mV Dropout

Power Supply 1: Linear Voltage Regulator

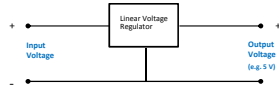
- Reduces the supply voltage to a stable value set value
 - Output voltage less than input voltage
 - A variable (controlled) resistor
- Key parameters
 - Output voltage (e.g. 5 V)
 - Input voltage range
 - Output current
 - Dropout
- E.g.: LM2940CT-5.0/NOPB
 - 5 Vout
 - 0V to 26V input
 - 1 A max output
 - 500mV Dropout




- E.g.: LM2940CT-5.0/NOPB
 - 5 Vout
 - 0V to 26V input
 - 1 A max output
 - 500mV Dropout

Power Supply II: Boost Converter

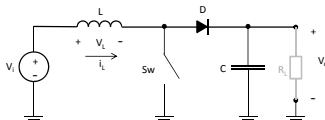- Used to boost the input voltage
- Uses a storage inductor as the storage element for the boost stage



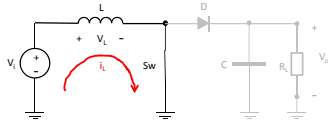Power Supply II: Boost Converter – 1 Charge Stage




- The switch is closed
- The inductor starts storing magnetic energy by conserving current passing through

$$\text{Voltage across an inductor: } V_L = L \frac{di_L}{dt}$$

$$\frac{V_L}{L} = \frac{di_L}{dt}$$

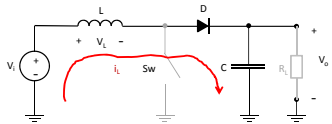
Power Supply II: Boost Converter – 2 Step-up Stage



- The switch opens
- Inductor "attempts" to maintain current and thus throws large inverted voltage to maintain current i_L .
- The current i_L passes through diode D and charges up capacitor C

Power Supply II: Boost Converter – LT1370

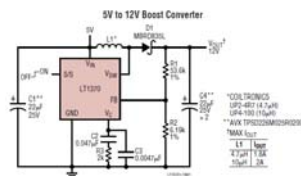
- Solid state solution switching regule
- Low (minimum) supply voltage 2.7 V
- Maximum 6A output current
- Typical application:
 - 12 V boost converter
- Use low ESR capacitors



Datasheet, LT1370, Linear Technology


Power Supply for Autonomous Car – Entire System

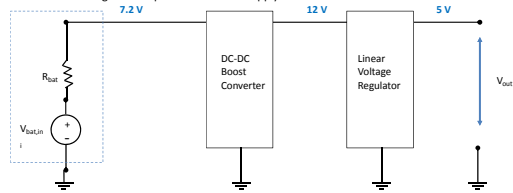- Two-component stable power-supply:
 - Boost converter to make sure input voltage to linear regulator is always $> 5\text{ V} + V_{\text{dropout}}$
 - E.g. 12 V
 - Linear regulator to provide stable 5 V supply




Power Supply for Autonomous Car – Entire System

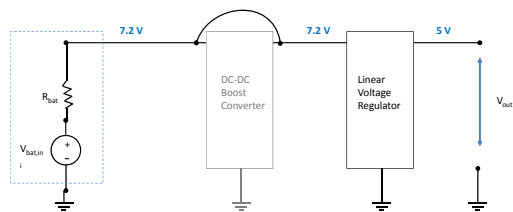- Redundancy:
 - Reliability through redundancy – can disconnect the DC-DC converter and still most likely be ok.
 - Can avoid high current conditions in SW




Power Supply for Autonomous Car – Entire System

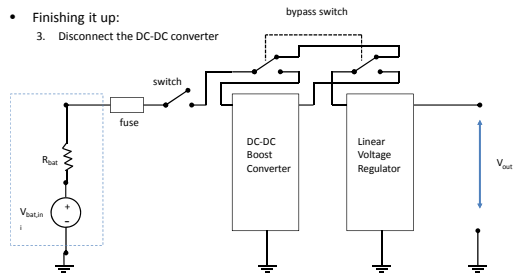- Finishing it up:
 - Disconnect the DC-DC converter



Sensors - An Introduction

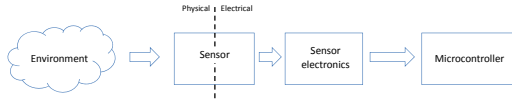- Obtains the information about the environment
- Provides transduction between the physical (mechanical) and electrical domains
 - Transduction: Conversion of energy between energy domains




Review – Operational Amplifiers

- Operational Amplifiers (OpAmps) are commonly used to amplify (precondition) sensing signal for input to a microcontroller

OpAmps are analyzed as *ideal*


Ideal OP-Amp: $V_{out} = A(V^+ - V^-)$

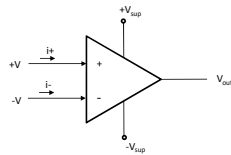- High input impedance ($i^+ \approx 0$, $i^- \approx 0$)
- Low output impedance
- Infinite gain (A is very large)




Review – Operational Amplifiers

- Two main configurations:

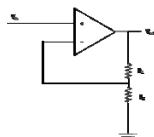


Non-inverting Amplifier

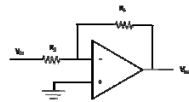

Inverting Amplifier

Review – Operational Amplifiers



- Inverting OpAmp as charge integrator

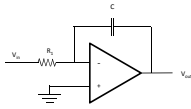

$$V_{out}(t) = - \int_0^t \frac{V_{in}(t)}{RC} dt + V_{out}(0)$$

Review – Operational Amplifiers

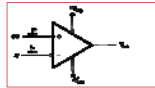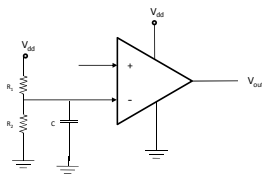- Single supply inverting OpAmp
 - Need to create a virtual ground at $\frac{1}{2} V_{dd}$



Summary: Sensors and Operational Amplifiers


- Sensors provide information about the state of the Environment to the microcontroller
- Operational Amplifiers (OpAmps) are often used to amplify the sensing signal
- OpAmps come in two flavors
 - Non-inverting
 - Inverting
- Gain of a non-inverting amplifier is always > 1
- A virtual ground can be used if an amplifier is used as single supply

Optical Rotary Encoders and Velocity Sensing

- Velocity sensing is necessary for a car to reach a set velocity
 - Recall $r \propto i_m$
 - To reach the desired velocity, the car has to accelerate, i.e. increase i_m
 - Once desired velocity is reached the car has to coast, reducing i_m to counteract friction and drag
 - i_m must be larger to maintain same velocity if traversing an incline
- Velocity = distance / time
- Assuming a no-slip condition:



$$\Delta x = \Delta \theta \cdot r$$
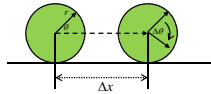
$$v = \frac{\Delta x}{\Delta t} = \frac{\Delta \theta}{\Delta t} \cdot r = \omega \cdot r$$





Optical Rotary Encoders and Velocity Sensing

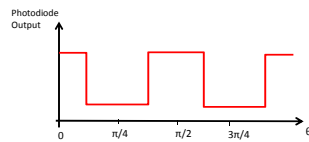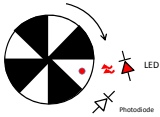- Optical Rotary Encoders:
 - Non-contact way to measure rotation/angular velocity
 - Can be purchased enclosed, or can be build onto the car wheel base
- Basics of operations:



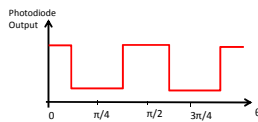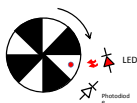Optical Rotary Encoders and Velocity Sensing



- Two ways to measure velocity:
 - Count number of transitions (edges) within a fixed amount of time.
 - Measure time between two transitions, i.e. the width of pulse or valley.
- Depends on the number of transitions v.s. sampling rate


Optical Rotary Encoders and Velocity Sensing

- Count number of edges in a fixed amount of time:

$$v = \frac{n \Delta \theta_{\text{enc}}}{t_s} \cdot r$$

where t_s is sampling time, n is the number of transitions, and $\Delta \theta_{\text{enc}}$ is the angle between transitions, in this case $\pi/4$.
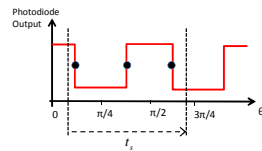
$$\text{Error: } \pm \frac{\Delta \theta_{\text{enc}}}{t_s} \cdot r$$



Optical Rotary Encoders and Velocity Sensing


- Measure time between transitions:

$$v = \frac{\Delta \theta_{\text{enc}}}{t_2 - t_1} \cdot r$$

where t_1 is the time of first transition, t_2 is the time of second transition. $\Delta \theta_{\text{enc}}$ is the angle between transitions, in this case $\pi/4$.


$$\text{Error: } \pm \frac{\Delta \theta_{\text{enc}}}{t_s} \cdot r$$

where t_s is the sampling interval.

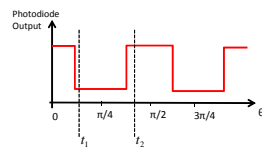

Velocity Sensing – Alternative Approaches

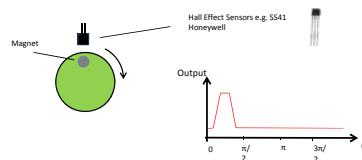- Optical encoder is just one way to measure velocity
- Other approaches include:
 - Back EMF from the motors
 - Other types of proximity sensors to mark a revolution of the wheel
 - Good example is Hall-effect sensors



Summary: Optical Rotary Encoders and Velocity Sensing

- Non-contact way of measuring rotation, can be integrated on the wheel
- Assuming no-slip conditions, wheel rotation corresponds to distance traveled
- An optical rotary encoder wheel can be used to measure rotation
- Two approaches:
 - Measure time between transitions
 - Count number of transitions within a time interval
 - Which approach to chose depends on: velocity, sampling time, allowable error
- Other approaches, such as sensing back EMF or hall effect (magnetic) sensing can be used to estimate the velocity

Optical Line Camera and Line Following

- A vision system is a key component in any autonomously driving car
- Optical camera projects an image onto a surface composed of light sensitive pixels
- Charge Coupled Device (CCD) image sensor:
 - An array of light sensitive pixels fabricated on a silicon chip, used to detect projected images
 - 2D array an essential component in many digital cameras
- Sophisticated image reconstruction algorithms usually need
- Line or edge following can be constructed using a 1D CCD array, and a simplified algorithm.



Optical Line Camera and Line Following

- Line camera contains
 - 1D CCD array (line)
 - Lens to focus the image across the CCD array
- Within the image plane
 - Image still projected on a plane
 - Only one line of image detected

